

# *Review of Circuit Theory*

## **A.1 Introduction**

Although this book minimizes math, some algebra is germane to the understanding of analog electronics. Math and physics are presented here in the manner in which they are used later, so no practice exercises are given. For example, after the voltage divider rule is explained, it is used several times in the development of other concepts, and this usage constitutes practice.

Circuits are a mix of passive and active components. The components are arranged in a manner that enables them to perform some desired function. The resulting arrangement of components is called a circuit or sometimes a circuit configuration. The art portion of analog design is developing the circuit configuration. There are many published circuit configurations for almost any circuit task, thus all circuit designers need not be artists.

When the design has progressed to the point that a circuit exists, equations must be written to predict and analyze circuit performance. Textbooks are filled with rigorous methods for equation writing, and this review of circuit theory does not supplant those textbooks. But, a few equations are used so often that they should be memorized, and these equations are considered here.

There are almost as many ways to analyze a circuit as there are electronic engineers, and if the equations are written correctly, all methods yield the same answer. There are some simple ways to analyze the circuit without completing unnecessary calculations, and these methods are illustrated here.

## **A.2 Ohm's Law**


Ohm's law is fundamental to all electronics. It can be applied to a single component, to any group of components, or to a complete circuit. When the current flowing through any portion of a circuit is known, the voltage dropped across that portion of the circuit is obtained by multiplying the current times the resistance (Eq. A.1).

$$V = IR \quad (\text{A.1})$$

The current (I) flows through the resistance (R), and the voltage (V) is dropped across R (Fig. A.1).



**Figure A.1**  
Ohm's law.

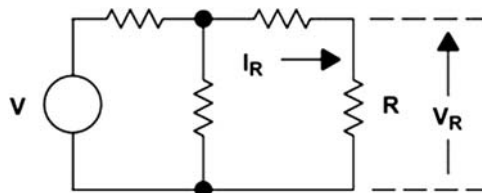

**Figure A.2**  
Ohm's law applied to a component.


In [Fig. A.2](#), Ohm's law is applied to a single component. The current ( $I_R$ ) flows through the resistor ( $R$ ) and the voltage ( $V_R$ ) is dropped across  $R$ . Notice, the same formula is used to calculate the voltage drop across  $R$  even though it is only a part of the circuit.

### ***A.3 Kirchhoff's Voltage Law***

Kirchhoff's voltage law states that the sum of the voltage drops in a series circuit equals the sum of the voltage sources. Otherwise, the source (or sources) voltage must be dropped across the passive components. When taking sums, keep in mind that the sum is an algebraic quantity. Kirchhoff's voltage law is illustrated in [Fig. A.3](#) and [Eqs. \(A.2\) and \(A.3\)](#).

$$\sum V_{\text{SOURCES}} = \sum V_{\text{DROPS}} \quad (\text{A.2})$$

$$V = V_{R1} + V_{R2} \quad (\text{A.3})$$

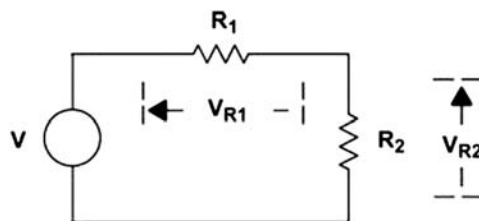

**Figure A.3**  
Kirchhoff's voltage law.

### A.4 Kirchhoff's Current Law

Kirchhoff's current law states: the sum of the currents entering a junction equals the sum of the currents leaving a junction. It makes no difference if a current flows from a current source, through a component, or through a wire, because all currents are treated identically. Kirchhoff's current law is illustrated in Fig. A.4 and Eqs. (A.4) and (A.5).

$$\sum I_{\text{IN}} = \sum I_{\text{OUT}} \quad (\text{A.4})$$

$$I_1 + I_2 = I_3 + I_4 \quad (\text{A.5})$$

### A.5 Voltage Divider Rule

When the output of a circuit is not loaded, the voltage divider rule can be used to calculate the circuit's output voltage. Assume that the same current flows through all circuit elements (Fig. A.5). Eq. (A.6) is written using Ohm's law. Eq. (A.7) is written as Ohm's law across the output resistor.


$$I = \frac{V}{R_1 + R_2} \quad (\text{A.6})$$

$$V_{\text{OUT}} = IR_2 \quad (\text{A.7})$$


Substituting Eq. (A.6) into Eq. (A.7), and using algebraic manipulation yields Eq. (A.8).

$$V_{\text{OUT}} = V \frac{R_2}{R_1 + R_2} \quad (\text{A.8})$$

A simple way to remember the voltage divider rule is that the output resistor is divided by the total circuit resistance. This fraction is multiplied by the input voltage to obtain the output voltage. Remember that the voltage divider rule always assumes that the output resistor is not loaded; the equation is not valid when the output resistor is loaded by a parallel component. Fortunately, most circuits following a voltage divider are input

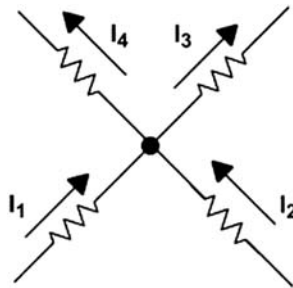

**Figure A.4**  
Kirchhoff's current law.

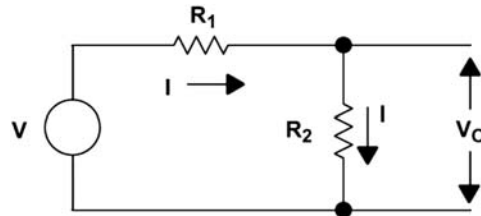

**Figure A.5**  
Voltage divider rule.

circuits, and input circuits are usually high resistance circuits. When a fixed load is in parallel with the output resistor, the equivalent parallel value comprised of the output resistor and loading resistor can be used in the voltage divider calculations with no error. Many people ignore the load resistor if it is 10 times greater than the output resistor value, but this will lead to a 10% error.

## A.6 Current Divider Rule

When the output of a circuit is not loaded, the current divider rule can be used to calculate the current flow in the output branch circuit ( $R_2$ ). The currents  $I_1$  and  $I_2$  in Fig. A.6 are assumed to be flowing in the branch circuits. Eq. (A.9) is written with the aid of Kirchhoff's current law. The circuit voltage is written in Eq. (A.10) with the aid of Ohm's law. Combining Eqs. (A.9) and (A.10) yields Eq. (A.11).


$$I = I_1 + I_2 \quad (\text{A.9})$$

$$V = I_1 R_1 = I_2 R_2 \quad (\text{A.10})$$

$$I = I_1 + I_2 = I_2 \frac{R_2}{R_1} + I_2 = I_2 \left( \frac{R_1 + R_2}{R_1} \right) \quad (\text{A.11})$$

Rearranging the terms in Eq. (A.11) yields Eq. (A.12).

$$I_2 = I \left( \frac{R_1}{R_1 + R_2} \right) \quad (\text{A.12})$$

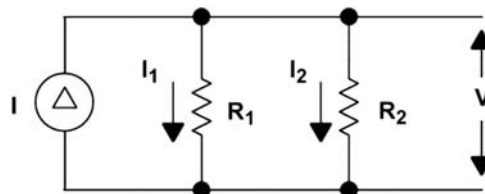

**Figure A.6**  
Current divider rule.

The total circuit current divides into two parts, and the resistance ( $R_1$ ) divided by the total resistance determines how much current flows through  $R_2$ . An easy method of remembering the current divider rule is to remember the voltage divider rule. Then modify the voltage divider rule such that the opposite resistor is divided by the total resistance, and the fraction is multiplied by the input current to get the branch current.


### A.7 Thevenin's Theorem

There are times when it is advantageous to isolate a part of the circuit to simplify the analysis of the isolated part of the circuit. Rather than write loop or node equations for the complete circuit, and solving them simultaneously, Thevenin's theorem enables us to isolate the part of the circuit we are interested in. We then replace the remaining circuit with a simple series equivalent circuit, thus Thevenin's theorem simplifies the analysis.

There are two theorems that do similar functions. The Thevenin's theorem just described is the first, and the second is called Norton's theorem. Thevenin's theorem is used when the input source is a voltage source, and Norton's theorem is used when the input source is a current source. Norton's theorem is rarely used, so its explanation is left for the reader to dig out of a textbook if it is ever required.

The rules for Thevenin's theorem start with the component or part of the circuit being replaced. Referring to Fig. A.7, look back into the terminals (left from C and  $R_3$  toward point XX in the figure) of the circuit being replaced. Calculate the no load voltage ( $V_{TH}$ ) as seen from these terminals (use the voltage divider rule).

Look into the terminals of the circuit being replaced, short independent voltage sources, and calculate the impedance between these terminals. The final step is to substitute the Thevenin's equivalent circuit for the part you wanted to replace as shown in Fig. A.8.

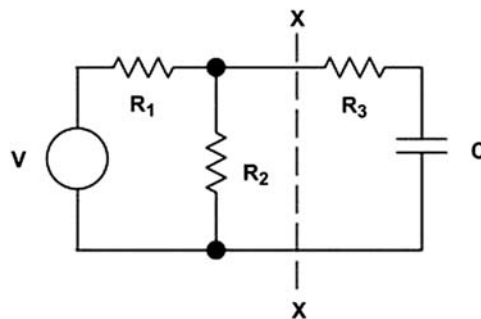

**Figure A.7**  
Original circuit.

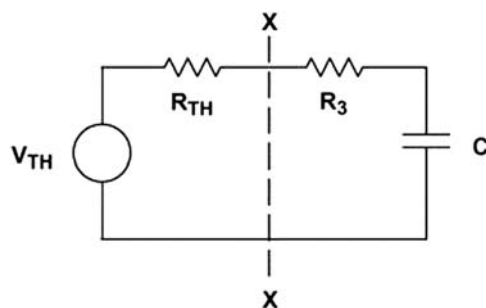


Figure A.8

Thevenin's equivalent circuit for Fig. A.7.

The Thevenin's equivalent circuit is a simple series circuit, thus further calculations are simplified. The simplification of circuit calculations is often sufficient reason to use Thevenin's theorem because it eliminates the need for solving several simultaneous equations. The detailed information about what happens in the circuit that was replaced is not available when using Thevenin's theorem, but that is no consequence because you had no interest in it.

As an example of Thevenin's theorem, let us calculate the output voltage ( $V_{OUT}$ ) shown in Fig. A.9A. The first step is to stand on the terminals X–Y with your back to the output circuit, and calculate the open circuit voltage seen ( $V_{TH}$ ). This is a perfect opportunity to use the voltage divider rule to obtain Eq. (A.13).

$$V_{TH} = V \frac{R_2}{R_1 + R_2} \quad (\text{A.13})$$

Still standing on the terminals X–Y, step two is to calculate the impedance seen looking into these terminals (short the voltage sources). The Thevenin impedance is the parallel impedance of  $R_1$  and  $R_2$  as calculated in Eq. (A.14). Now replace the circuit to the left of X–Y with the Thevenin's equivalent circuit  $V_{TH}$  and  $R_{TH}$ .

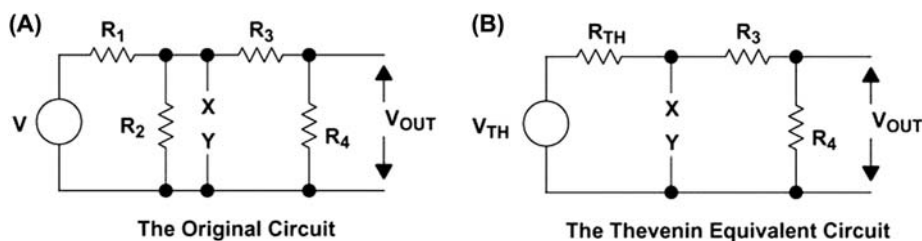


Figure A.9

Example of Thevenin's equivalent circuit. (A) The original circuit (B) the Thevenin's equivalent circuit.

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2 \quad (\text{A.14})$$

Note: Two parallel vertical bars ( $\parallel$ ) are used to indicate parallel components as shown in Eq. (A.14).

The final step is to calculate the output voltage. Notice the voltage divider rule is used again. Eq. (A.15) describes the output voltage, and it comes out naturally in the form of a series of voltage dividers, which makes sense. That is another advantage of the voltage divider rule; the answers normally come out in a recognizable form rather than a jumble of coefficients and parameters.

$$V_{OUT} = V_{TH} \frac{R_4}{R_{TH} + R_3 + R_4} = V \left( \frac{R_2}{R_1 + R_2} \right) \frac{R_4}{\frac{R_1 R_2}{R_1 + R_2} + R_3 + R_4} \quad (\text{A.15})$$

The circuit analysis is done the hard way in Fig. A.10, so you can see the advantage of using Thevenin's theorem. Two loop currents,  $I_1$  and  $I_2$ , are assigned to the circuit. Then the loop Eqs. (A.16) and (A.17) are written.

$$V = I_1(R_1 + R_2) - I_2 R_2 \quad (\text{A.16})$$

$$I_2(R_2 + R_3 + R_4) = I_1 R_2 \quad (\text{A.17})$$


Eq. (A.17) is rewritten as Eq. (A.18) and substituted into Eq. (A.16) to obtain Eq. (A.19).

$$I_1 = I_2 \frac{R_2 + R_3 + R_4}{R_2} \quad (\text{A.18})$$

$$V = I_2 \left( \frac{R_2 + R_3 + R_4}{R_2} \right) (R_1 + R_2) - I_2 R_2 \quad (\text{A.19})$$

The terms are rearranged in Eq. (A.20). Ohm's law is used to write Eq. (A.21), and the final substitutions are made in Eq. (A.22).

$$I_2 = \frac{V}{\frac{R_2 + R_3 + R_4}{R_2} (R_1 + R_2) - R_2} \quad (\text{A.20})$$

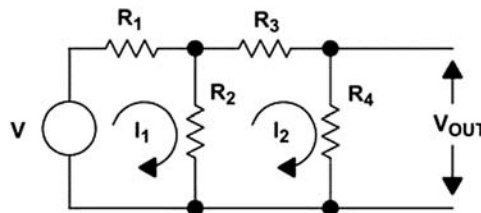

**Figure A.10**

Analysis done the hard way.

$$V_{OUT} = I_2 R_4 \quad (A.21)$$


$$V_{OUT} = V \frac{R_4}{\frac{(R_2 + R_3 + R_4)(R_1 + R_2)}{R_2} - R_2} \quad (A.22)$$

This is a lot of extra work for no gain. Also, the answer is not in a usable form because the voltage dividers are not recognizable, thus more algebra is required to get the answer into usable form.


## A.8 Superposition

Superposition is a theorem that can be applied to any linear circuit. Essentially, when there are independent sources, the voltages and currents resulting from each source can be calculated separately, and the results are added algebraically. This simplifies the calculations because it eliminates the need to write a series of loop or node equations. An example is shown in Fig. A.11.

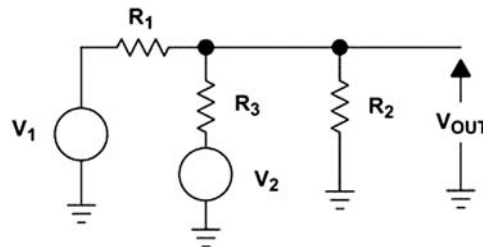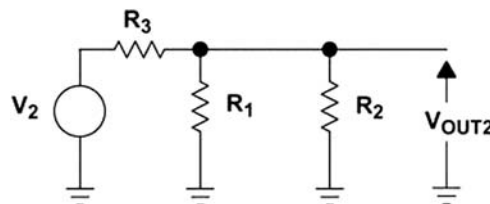When  $V_1$  is grounded,  $V_2$  forms a voltage divider with  $R_3$  and the parallel combination of  $R_2$  and  $R_1$ . The output voltage for this circuit ( $V_{OUT2}$ ) is calculated with the aid of the voltage divider Eq. (A.23). The circuit is shown in Fig. A.12. The voltage divider rule yields the answer quickly.

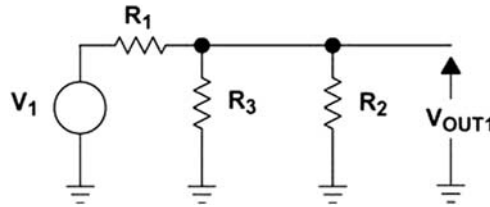


**Figure A.11**  
Superposition example.



**Figure A.12**  
When  $V_1$  is grounded.



**Figure A.13**When  $V_2$  is grounded.

$$V_{OUT2} = V_2 \frac{R_1 \parallel R_2}{R_3 + R_1 \parallel R_2} \quad (\text{A.23})$$

Likewise, when  $V_2$  is grounded (Fig. A.13),  $V_1$  forms a voltage divider with  $R_1$  and the parallel combination of  $R_3$  and  $R_2$ , and the voltage divider theorem is applied again to calculate  $V_{OUT}$  (Eq. A.24).

$$V_{OUT1} = V_1 \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} \quad (\text{A.24})$$

After the calculations for each source are made the components are added to obtain the final solution (Eq. A.25).

$$V_{OUT} = V_1 \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} + V_2 \frac{R_1 \parallel R_2}{R_3 + R_1 \parallel R_2} \quad (\text{A.25})$$

The reader should analyze this circuit with loop or node equations to gain an appreciation for superposition. Again, the superposition results come out as a simple arrangement that is easy to understand. One looks at the final equation and it is obvious that if the sources are equal and opposite polarity, and when  $R_1 = R_3$ , then the output voltage is zero.

Conclusions such as this are hard to make after the results of a loop or node analysis unless considerable effort is made to manipulate the final equation into symmetrical form.